

Project Title:

3-Bit Password Checker (Digital Lock)

Student Name:


Oluwapelumi Adewuyi

Boolean Expression Used:

$$F(A, B, C) = A \cdot B' \cdot C$$

Truth Table:

A	B	C	F(UNCLOCKED)
0	0	0	0
0	1	0	0
0	1	1	1
0	0	0	1
0	0	1	1
1	1	1	1

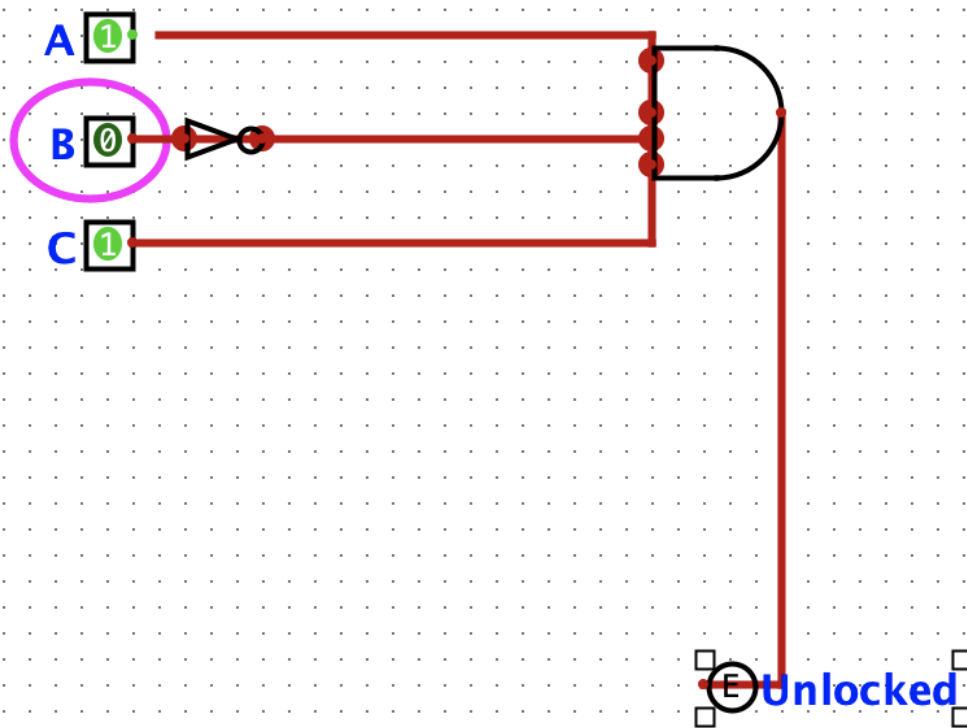

**Brief Description:**

This circuit simulates a basic password-activated lock system using digital logic gates. It uses a NOT gate to invert the B input and a 3-input AND gate to evaluate the condition  $A = 1$ ,  $B = 0$ , and  $C = 1$ . The “Unlocked” output only goes high when the exact binary input 101 is entered.